

LinearAmplifiers

October 30, 2018

1 Linear applications of operational amplifiers

In this example a TL082 operational amplifier was used. The input signal was set to a sine wave of 10 mV amplitude and 10 kHz frequency with additional gaussian noise.

$$E_g = A \sin(\omega t) + \alpha N(t)$$

$$\omega = 2\pi f$$


```
In [2]: using PyPlot;
```

```
In [3]: # system definition for TL082
```

```
Aol = 100/0.001      # 80 dB
ft = 4*10^6;         # 4 MHz
Rinr = 10^12;        # input resistance
CMRR = 100           # Common Mode Rejection Ratio
PSRR = 100           # Power Supply Rejection Ratio
Vn = 25*10^(-9);     # Input noise voltage
SR = 13*10^(6);      # Slew Rate

A = 0.01;            # amplitude
f = 10^4;            # frequency 10 kHz
alfa = 0.0050;       # noise amplitude
t = 0:0.00001:0.001; # 1 ms time vector with a resolution of 10 us
E = A*sin.(2 *pi * f *t) + alfa*rand(length(t),1); # sinusoidal signal definition
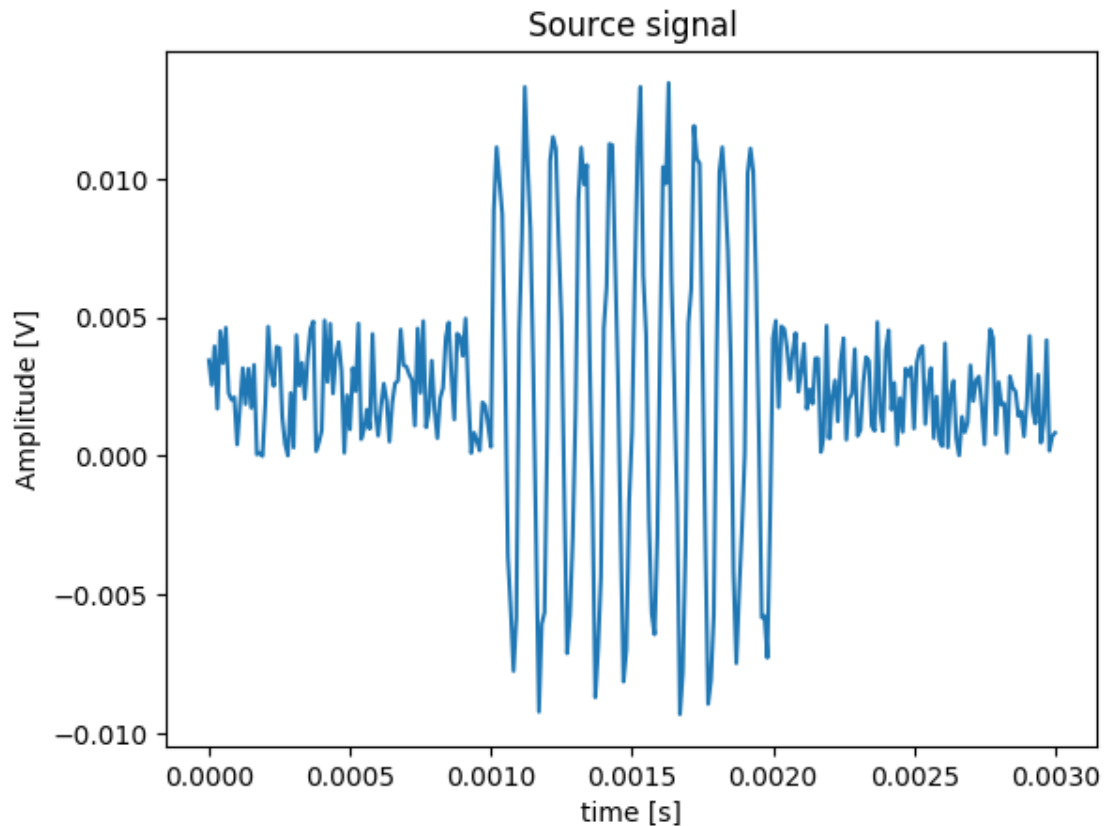
# add noise in front and at the back of the sine signal
Eg = [alfa*rand(100,1); E; alfa*rand(100,1)];
t = 0:0.00001:0.003;
Rg = 500;            # signal source thevenin impedance
plot(t,Eg)
title("Source signal")
xlabel("time [s]");
ylabel("Amplitude [V]");
```



1.1 Inverting amplifier

$$A_V = -\frac{R_f}{R_{in}}$$

```
In [4]: # External resistors
Rin = 1000;
Rf = 10000;
println("The value to Rin is $Rin Ohm")
println("The value to Rin is $Rf Ohm")
Av = -Rf/Rin;
AvdB = floor(20log10.(abs(Av)))
println("The value of the voltage gain is $Av V/V, what is equal to $AvdB dB")
Rin = Rin;
println("The input resistance of the inverting amp is equal to $Rin");
```


The value to Rin is 1000 Ohm

The value to Rin is 10000 Ohm

The value of the voltage gain is -10.0 V/V, what is equal to 20.0 dB

The input resistance of the inverting amp is equal to 1000
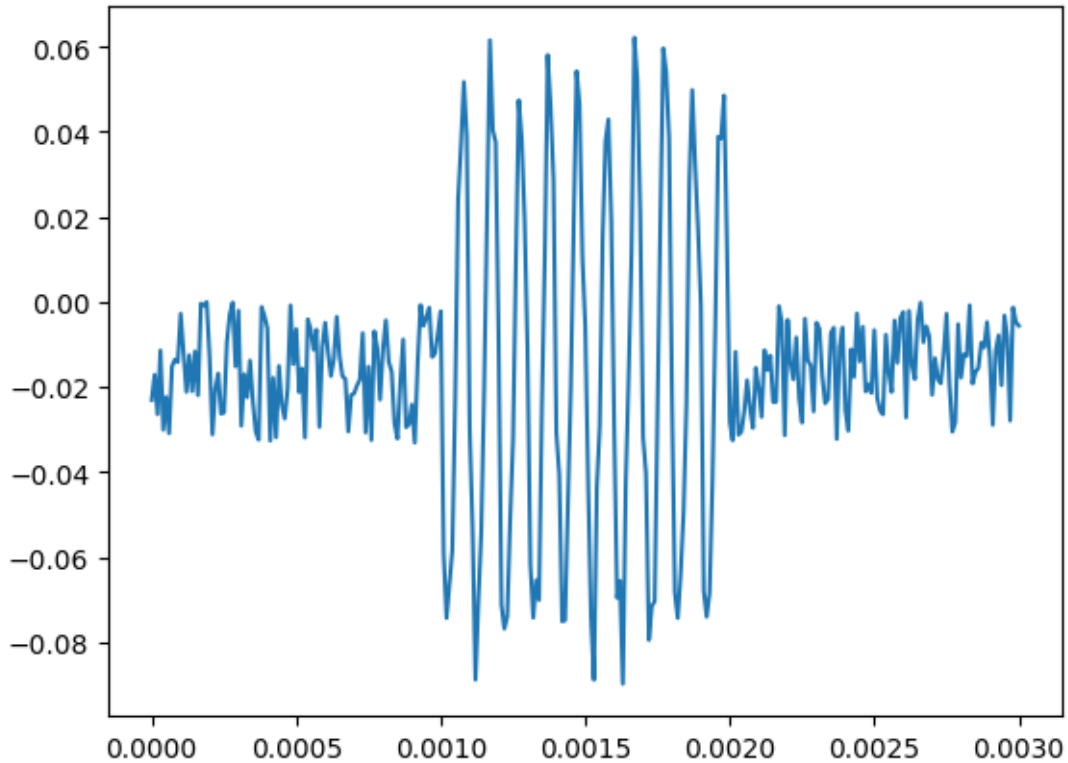
```
In [5]: Rin = Rin;
        R1 = Rin;
        R2 = Rf;
        Vout = Av * Eg * Rin/(Rin + Rg);
        plot(t,Vout)
```



```
Out[5]: 1-element Array{PyObject,1}:
         PyObject <matplotlib.lines.Line2D object at 0x7f43d6b8f290>
```

Gain Bandwidth

$$GB = f_T = A_v \cdot f$$

```
In [6]: fc = ft/abs(Av);
        fc = round(fc/1000);
        println("The cut off frequency is equal to $fc [kHz]")
```

The cut off frequency is equal to 400.0 [kHz]


1.1.1 Non inverting amplifier

$$A_v = 1 + \frac{R_2}{R_1}$$

```
In [7]: Av = 1 + R2/R1;
        AvdB = round(20*log10.(abs(Av)));
        println("The value to the voltage gain is $Av V/V, what is equal to $AvdB dB");
```

The value to the voltage gain is 11.0 V/V, what is equal to 21.0 dB
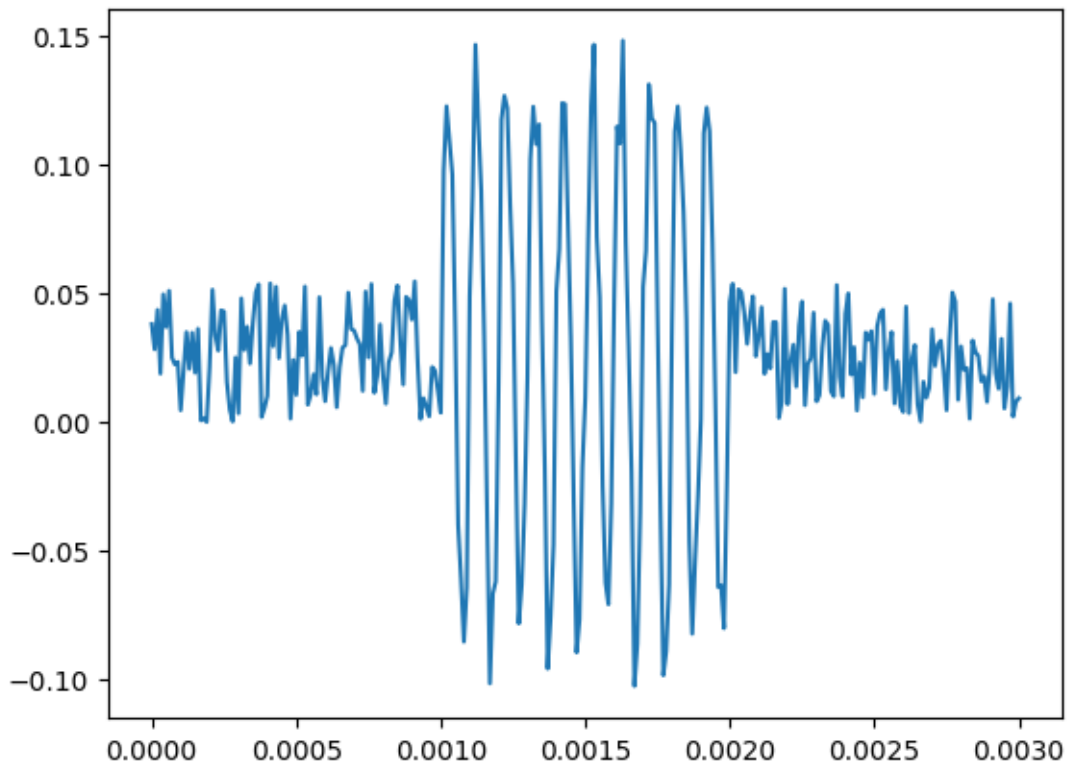
```
In [8]: Rin = Rinr + R1*R2/(R1+R2) ; # input resistance
        println("The input resistance of the non inverting amp is equal to $Rin");
        Vout = Av * Eg * Rin/(Rin + Rg) ;
        plot(t,Vout)
```



The input resistance of the non inverting amp is equal to 1.000000000909091e12

```
Out[8]: 1-element Array{PyObject,1}:
        PyObject <matplotlib.lines.Line2D object at 0x7f43d6b0f590>
```

```
In [9]: fc = ft/Av;
        fc = round(fc/1000);
        println("The cut off frequency is equal to $fc [kHz]")
```

The cut off frequency is equal to 364.0 [kHz]


1.2 Summing Amp

$$V_{out} = - \sum_{k=1}^N \frac{R_f}{R_i} V_i$$

In []:

```
In [10]: A = 0.01;                # amplitude
         f = 10^4;                # frequency 10 kHz
         alfa = 0.0001;           # noise amplitude
         t = 0:0.00001:0.001;    # 1 ms time vector with a resolution of 10 us
         E = A*sin.(2 *pi * f *t) + alfa*rand(length(t),1); # sinusoidal signal definition

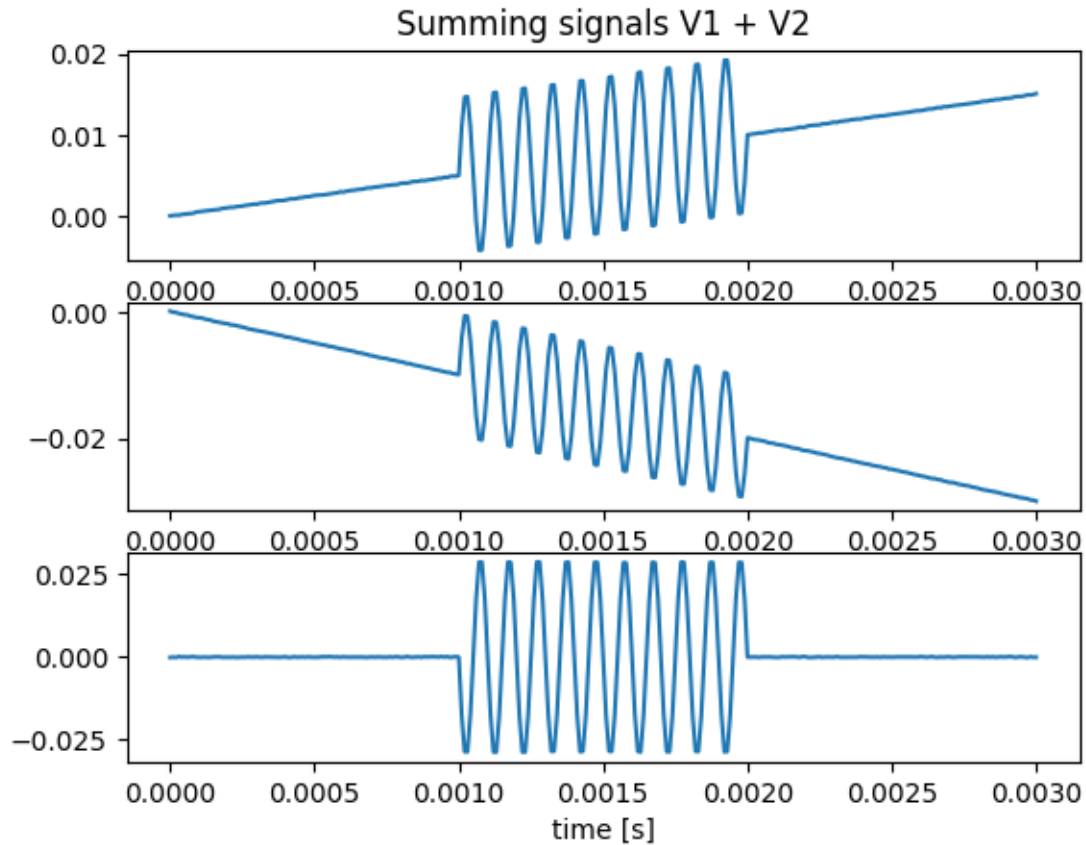         # add noise in front and at the back of the sine signal
         V1 = [alfa*rand(100,1); E; alfa*rand(100,1)];
         V2 = [alfa*rand(100,1); E; alfa*rand(100,1)];
         t = 0:0.00001:0.003;
         V1 = 5*t + V1;
         V2 = -10*t + V2;
         V = -(2*V1+V2);
         Rg = 500;                # signal source thevenin impedance
         subplot(3,1,1); plot(t,V1)
         title("Summing signals V1 + V2")
         subplot(3,1,2); plot(t,V2)
         subplot(3,1,3); plot(t,V)
         xlabel("time [s]");
```



1.3 Integrator circuit

$$V_{out} = -\frac{1}{RC} \int_{t_0}^{t_1} V_{in} dt = K_i \int_{t_0}^{t_1} V_{in} dt$$

```
In [11]: R = 10000;
C = 10^(-8);
Ki = -1/(R*C);
println("Integration constant = $Ki");
```

Integration constant = -9999.999999999996

1.3.1 Example

$$V_{out} = -\frac{1}{RC} \int_{t_0}^{t_1} V_{in} dt = -K_i \int_{t_0}^{t_1} V_{in} dt$$

$$V_{in}(t) = \begin{cases} A & t \in (kT, kT + \tau) \\ -A & t \in (kT + \tau, kT + T) \end{cases}$$

$$\begin{aligned}
\int_{t_0}^T V_{in}(t)dt &= \int_{t_0}^{\tau} V_{in}(t)dt + \int_{\tau}^T V_{in}(t)dt \\
\int_{t_0}^{\tau} V_{in}(t)dt + \int_{\tau}^T V_{in}(t)dt &= \int_{t_0}^{\tau} A dt + \int_{\tau}^T -A dt \\
\int_{t_0}^{\tau} A dt + \int_{\tau}^T -A dt &= A t|_{t_0}^{\tau} - A t|_{\tau}^T \\
-K_i \int_{t_0}^{\tau} A dt + -K_i \int_{\tau}^T -A dt &= -K_i A t|_{t_0}^{\tau} + K_i A t|_{\tau}^T
\end{aligned}$$

```

In [12]: A = 0.5;
         f = 100;
         T = 1/f;
         tau = 0.5*T;

         #for positive amplitude
         min = A*Ki*tau;
         # for negative amplitude
         max = -A*Ki*T - (-A*Ki*tau);

```

```


In [13]: t1 = 0:0.01*tau:tau;
         t2 = tau:0.01*tau:T;
         t = [t1; t2];

         x1 = A*ones(length(t1),1 );
         x2 = -A*ones(length(t2),1 );
         x = [x1; x2]

         y1 = A*Ki*t1;
         y2 = -A*Ki*t2;
         y2 = y2.-2*max;
         y = [y1; y2]

         subplot(2,1,1); plot(1000*t,x)
         subplot(2,1,2); plot(1000*t,y)
         xlabel("time [ms]");

```

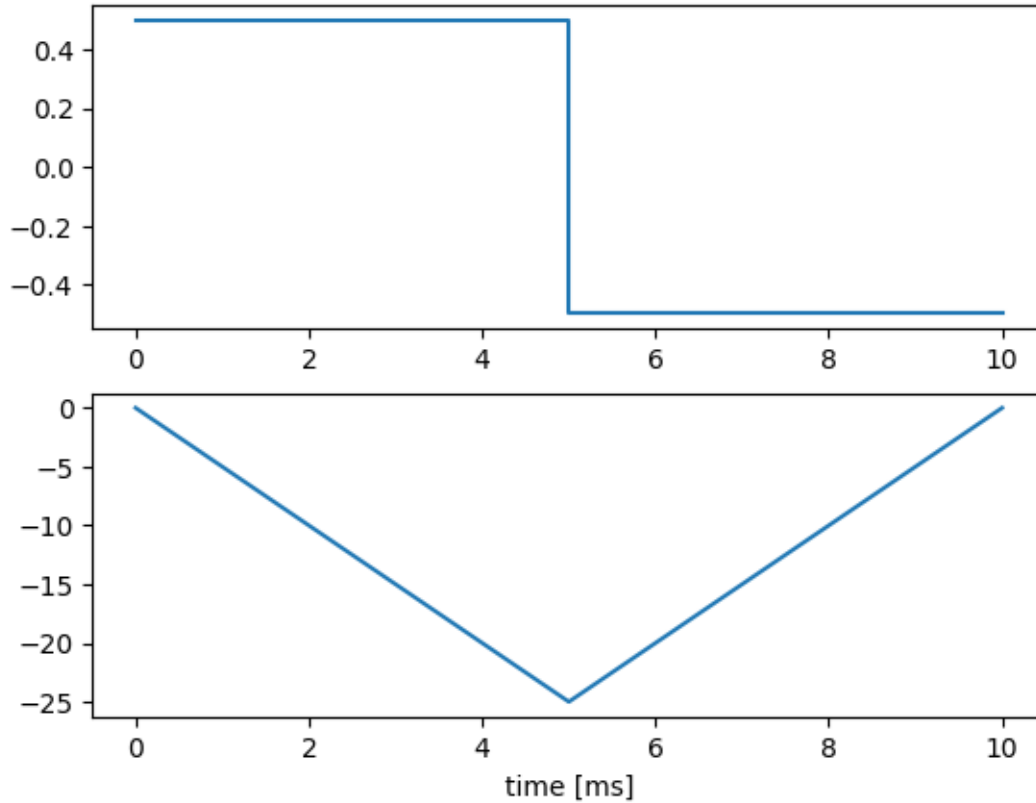

1.4 Derivative circuit

$$V_{out}(t) = -RC \frac{dV_{in}(t)}{dt}$$

1.4.1 Example

Triangular wave derivative

$$V_{in}(t) = \begin{cases} \alpha t & t \in (kT, kT + \tau) \\ -\alpha t & t \in (kT + \tau, kT + T) \end{cases}$$

```
In [14]: T = 0.001;
        tau = 0.5*T
        f = 1/T;
        R = 10000; # 10k
        C = 10*10^(-9); # 10n
        Kd = -R*C;
        println("Derivation constant = $Kd");
        A = 10;
        alpha = A/(0.25*T);
        println("Slope = $alpha");
```



```
sol = -Kd*d;  
println("Solution Kd*d = $sol [V]");
```

```
Derivation constant = -0.000100000000000000005  
Slope = 40000.0
```

```
UndefVarError: d not defined
```

```
Stacktrace:
```

```
[1] top-level scope at In[14]:11
```

```
In [ ]:
```

```
In [ ]:
```